



Science

1. Complete the table.

Circuit symbol	Name
	
	wire
	bulb
	

2. Will these circuits work? Explain your answers.

